

2016

PHYSICS

(Major)

Paper : 3.2

(**Current Electricity and Magnetostatics**)

Full Marks : 60

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Answer the following questions : 1×5=5

- (a) The coefficient of coupling between two coils is 0.6. What does it mean?
- (b) State Ampere's circuital law for steady currents.
- (c) How does a current loop behave as a magnetic dipole?

- (d) When does a series L - C - R circuit have the maximum impedance and what is its value?
- (e) A transformer cannot work on d.c. Explain why.

2. Answer the following questions : 2×5=10

- (a) Why is Wheatstone bridge not suitable for measurement of very low resistance?
- (b) What do you mean by Q factor of an a.c. series resonant circuit?
- (c) In a region, the force $\vec{F} = q(\vec{v} \times \vec{B})$ on a charge q is zero. What conclusions can you draw from it?
- (d) Explain the differences between a 'dead-beat' galvanometer and a 'ballistic' galvanometer.
- (e) Establish that

$$i = \int_S \vec{J} \cdot \hat{n} dA$$

where \hat{n} is a unit vector normal to the area dA .

(7)

Or

- (a) "Divergence of magnetic field is zero whereas divergence of electric field is not zero."

What meaning will you derive about the two fields from the above statement? 3

- (b) A rectangular current loop is suspended in a uniform magnetic field. Obtain an expression for the torque on the loop. 7
